
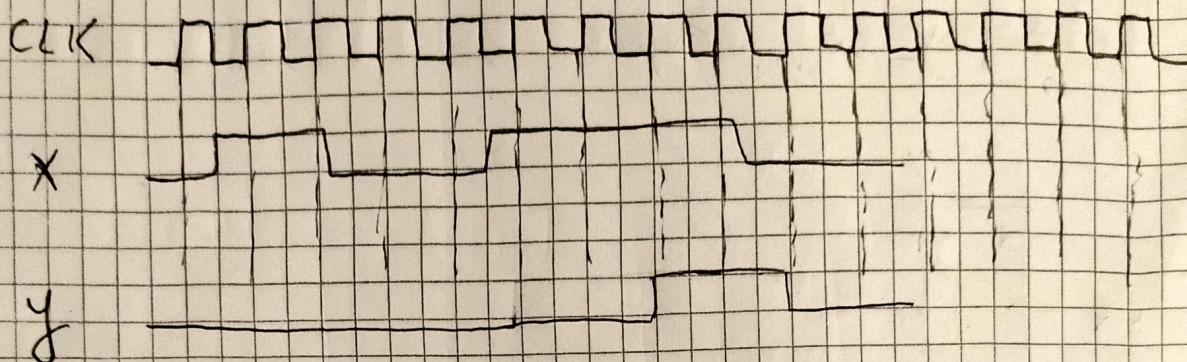


1- Diagrama de tiempos

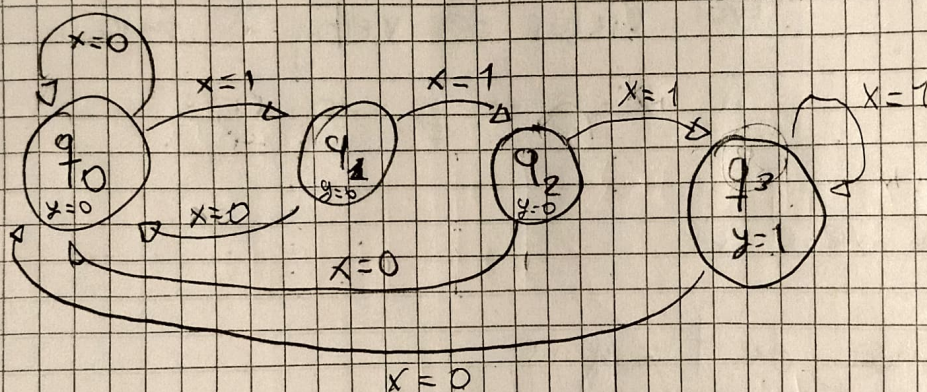

2- Diagrama de estados



3- Table de estado - salida

Estado actual (EA)	Estado sig.		Salida Z	
	x=0	x=1	x=0	x=1
q ₀	q ₀	q ₁	0	0
q ₁	q ₀	q ₂	0	0
q ₂	q ₀	q ₃	0	0
q ₃	q ₀	q ₃	1	1

4- Asignación de Estados

	Q_1	Q_2
$q_0 -$	0	0
$q_1 -$	0	1
$q_2 -$	1	0
$q_3 -$	1	1

5 - Tabla de estados - salidas

Actual $Q_1[n] \mid Q_0[n]$		$Q_1[n+1]$		$Q_0[n+1]$		Y	
		$X=0$	$X=1$	$X=0$	$X=1$	$X=0$	$X=1$
q_0	0 0	0	0	0	1	0	0
q_1	0 1	0	1	0	0	0	0
q_2	1 0	0	1	0	1	0	0
q_3	1 1	0	1	0	1	1	1

6) Logica de estado siguiente

$$D[n+1] = D$$

Nota: volver al paso anterior si no entiende

D_1 :

$D_1[n]$	$D_0[n]$	x	D_1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

x	D_1, D_0			
	00	01	11	10
0	0	0	0	0
1	0	1	1	1

$$D_1[n+1] = D_1 = (x D_0) + (x D_1)$$

D_0 :

$D_1[n]$	$D_0[n]$	x	$D_0 = D_0[n+1]$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

x	D_1, D_0			
	00	01	11	10
0	0	0	0	0
1	1	0	1	1

$$D_0[n+1] = (x \overline{D_0}) + (x D_1)$$

Flex

Papiro

7)

Tabla de Salida

Q_1	Q_0	x	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$Q_1 \backslash Q_0$	00	01	11	10
0	0	0	1	0
1	0	0	1	0

 $y = Q_1 \cdot Q_0$